

## **Comparison of Node-Voltage and Mesh-Current Analytical Techniques**

### **Active Learning Example for Circuits VCP**

**Overview:** When introduced to the different analytical techniques, students may not see the advantage of one method versus another. Often, students will adopt a 'favorite' method and always use that one, regardless of the circuit layout. In this activity students will identify key differences between two methods, and which method may be more advantageous given a particular circuit. Perhaps even more importantly, by the end of the activity, they will learn to *think* about the circuit before “jumping right in” and analyzing it.

**Summary of Activity:** Students are asked to work in pairs and groups of 4 to analyze resistive dc circuits using two different methods (Node-Voltage Analysis and Mesh-Current Analysis). Upon completion of the activity, they should be able to better judge which technique is most appropriate to use given a particular circuit.

*Appropriate audience:* This activity would be appropriate after the Node-Voltage and Mesh-Current analytical techniques have been introduced and the students have had some practice applying both techniques, but likely not proficient at them.

#### **Activity (Groups of 4):**

Students are presented with two circuits, Circuit 1 and Circuit 2 (*Example circuits are shown on the next page*).

Students A and B work together, using Mesh-Current Analysis on both Circuit 1 and Circuit 2 to determine the voltage at each node and the current through each of resistors.

Students C and D work together, using Node-Voltage Analysis on both Circuit 1 and Circuit 2 to determine the voltage at each node and the current through each of resistors.

After analyzing the circuits, the four students gather together to share their results. They should:

- 1) Determine if they calculated the same voltage values and current values.
- 2) Determine which method they have the most confidence in for each circuit, if they have different results (likely more confidence in Node-Voltage Analysis for Circuit 1 and Mesh-Current Analysis for Circuit 2 since values are 'known?') (*instructor may want to provide the correct values at this point*)
- 3) Discuss which method was "easier" for each circuit - and **WHY** that might be.

After they have discussed amongst themselves, instructor can lead a discussion about the characteristics of each circuit, and solicit ideas on why one technique was easier/better than the other. Try to identify key properties for each circuit. After the properties are

identified, the students are given two additional circuits (Circuits 3 and 4) with a mixture of voltage and current sources.

As a group (of 4), the students should quickly determine which technique they believe will be best for Circuit 3 and which technique will be best for Circuit 4.


Students A & B, working together, develop the Node-Voltage equations for both circuits. Students C & D, working together, develop the Mesh-Current equations for both circuits.

*-if time allows, you can have them calculate the actual voltages and currents in the circuit*


Again, the students gather as a group of 4 to discuss their results and answer:

- Were their predictions correct (which technique was best for each circuit)?
- If not, what might their prediction have been wrong?
- If yes, will their line of thinking extend to any circuit?


Instructor can again lead a discussion as to which circuit properties are the most helpful in determining the appropriate analytical technique to employ, based on the student experience.

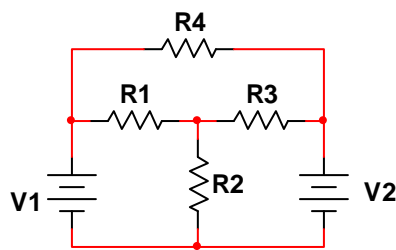


**Circuit 1**

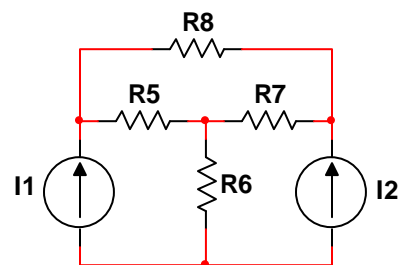

**Circuit 2**

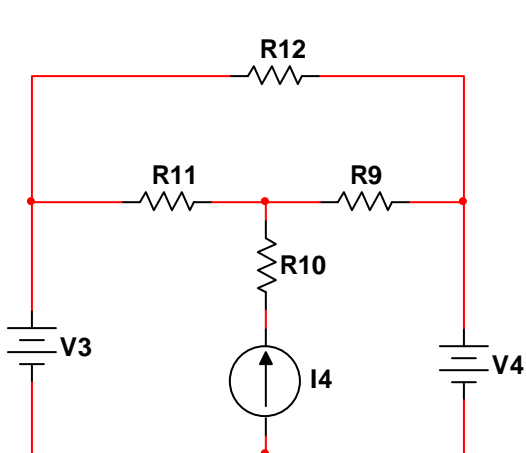

**Circuit 3**

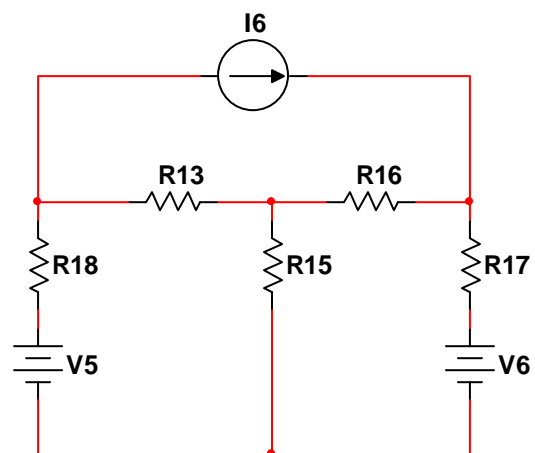

**Circuit 4**