

## FINAL EXAM

**Dec 16<sup>th</sup> , 2013, 10:30am-1:15pm**

**Honor pledge: "On my honor I have neither given nor received aid on this exam."**

**Name:** \_\_\_\_\_ **Signature:** \_\_\_\_\_

- **Calculators allowed.**
- **Single sided 8.5x11 sheet with formulas and circuits allowed.**
- No books, no cell phones allowed.
- Write in English. Write clearly. Write neatly.
- All your answers must be in these stapled pages. If you use the backside you need to indicate this on the front. Back of pages are usually **NOT** graded.
- Do not take the staple off.
- Do not expect the answers to be integers.


For this exam please assume, unless otherwise specified, that:

- Voltages are measured in reference to ground.
- Light bulbs are resistances.
- All switches are actuated in the direction shown by their arrows at  $t=0s$ , unless otherwise noted by the switch.
- Operational amplifiers are properly powered, so that they don't saturate.


Question	Max points	Grade
1	2	
2	2	
3	2	
4	2	
5	1	
6	1	
7	20	
8	20	
9	20	
10	20	
11	5	
12	5	
total		

- Which of the following graphs shows the natural response of an RLC circuit that is underdamped?
  - Graph 1
  - Graph 2
  - Graph 3
  - Either graph 1 or 2
  - None of the above


Graph 1:

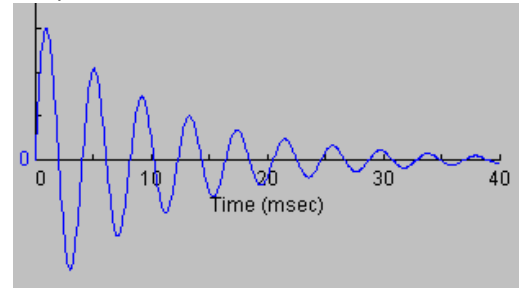

Graph 2:


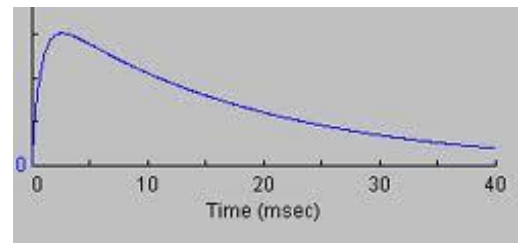


Graph 3:

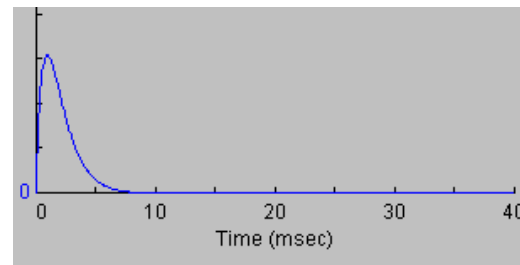


- A light bulb is connected to a voltage supply and lights up. When a second one is connected in series to the first one:
  - Current through the first one will go up.
  - This won't work, as light bulbs need to always be connected in parallel.
  - Required power from the supply will go up.
  - Current through the first one will go down.
  - None of the above.
- This question refers to the figure with the resistors and voltage supplies. The voltage measured by a multimeter connected to node 2, in reference to node 1, is:
  - 0V
  - 4V
  - 2V
  - 3V
  - 4V
- Referring still to the same circuit, if node 2 is shorted to ground, the voltage on node 1, in reference to ground:
  - Doesn't change.
  - Goes to zero.
  - Changes to 1V.
  - Goes to 3V.
  - None of the above.

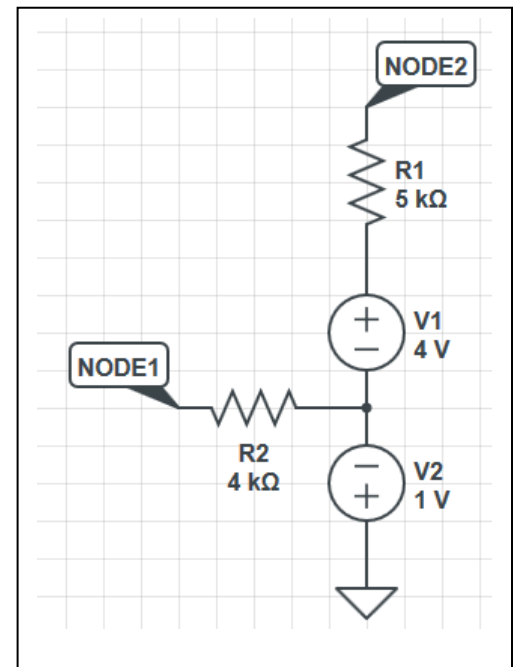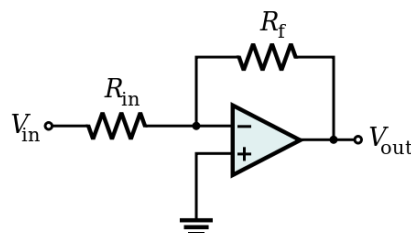
- On the figure with the opamp,  $R_f=1k\ \Omega$  and  $R_{in}=500\ \Omega$ . If  $V_{in}$  is 0.5V, what is  $V_{out}$ ?
  - 2V
  - 1V
  - 2V
  - 1V
  - none of the above



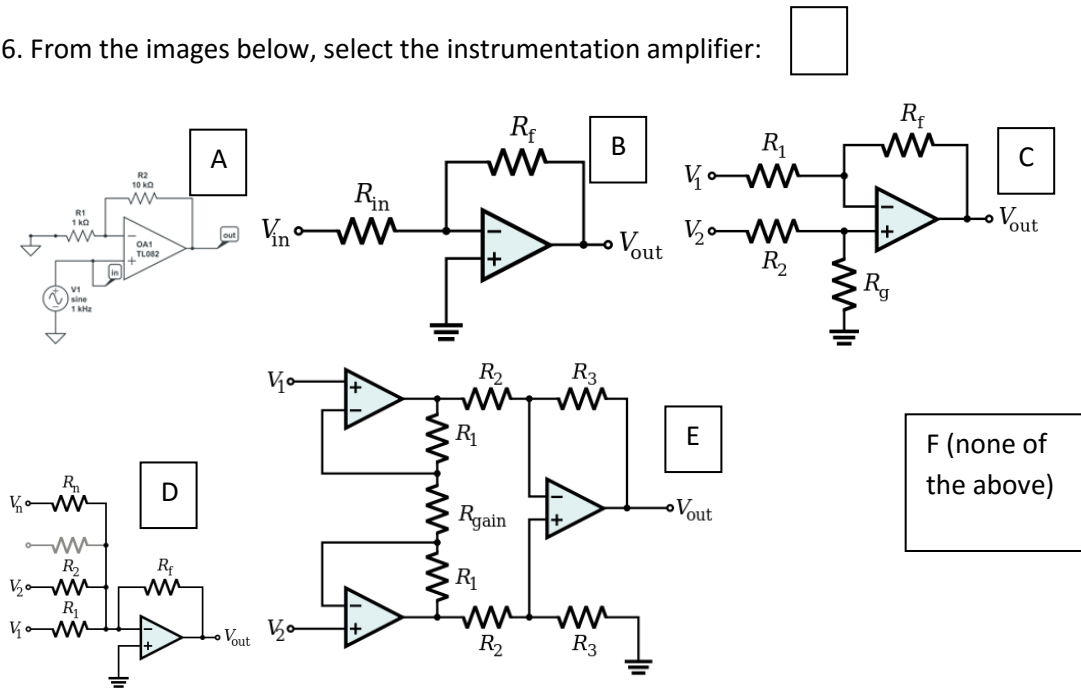
6. From the images below, select the instrumentation amplifier:



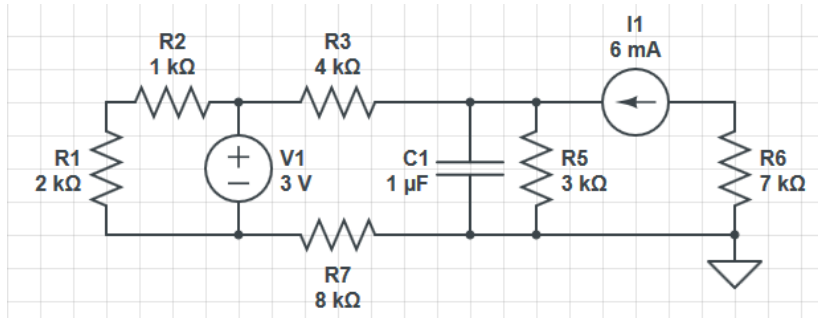7. Find the Thévenin equivalent from the perspective of the capacitor. (Hint: source transformation won't work here.) You can use any method you would like. Consider superposition one of them.




TEC:

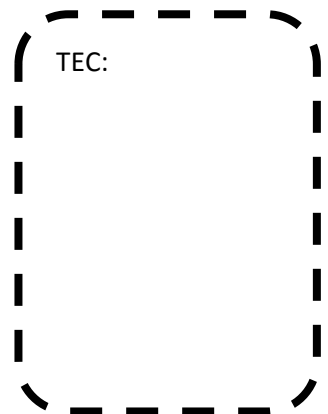


8. Find the nodal voltage  $V_2$  for  $t \geq 0$ .

$V_2 =$

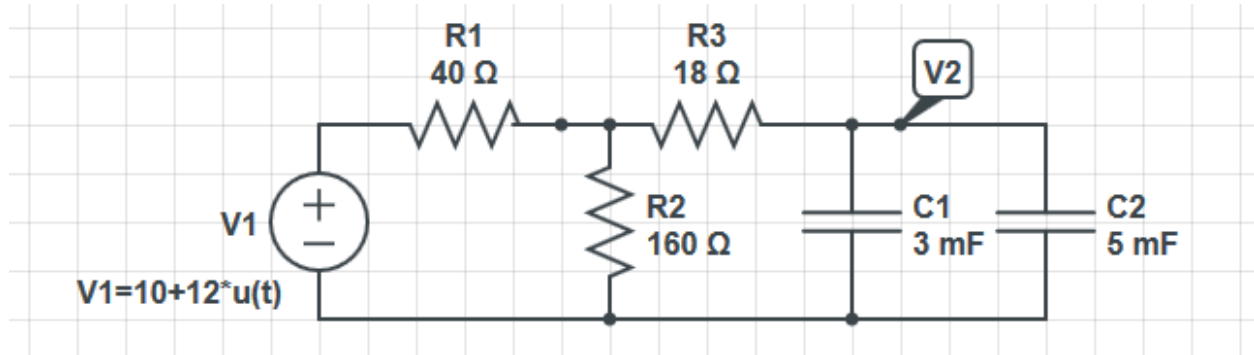


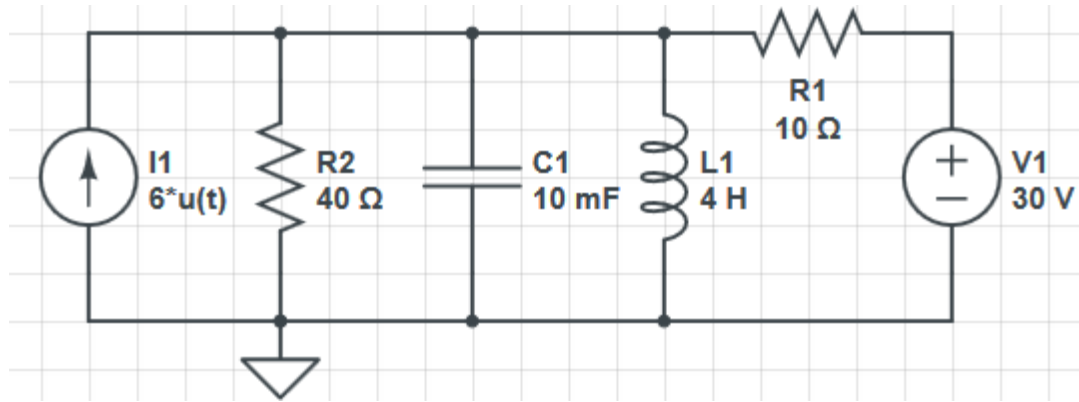9. a) Find the current through the inductor for  $t \geq 0$ . (8pts)  
b) Find the voltage across the capacitor for  $t \geq 0$ . (7 pts)  
c) Find the energy stored in both (L and C) at  $t=100\text{ms}$ . (5 pts)



$i(t) =$   
 $v(t) =$   
 $w1 =$   
 $w2 =$

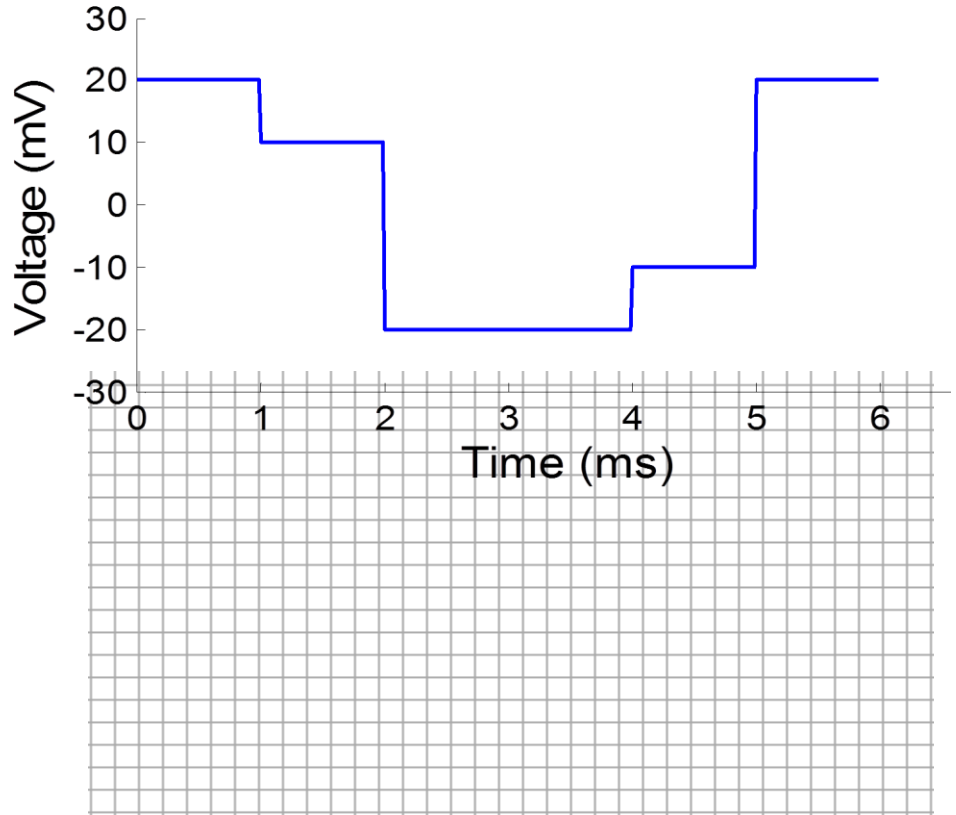10. (a) An op amp integrator with  $R=4M\Omega$  and  $C=1\ \mu\text{F}$  is properly powered so that it doesn't saturate for the input given below. Sketch the output. (10 pts)





10 (b) Plot the output of the circuit below, given the input is a triangular wave with amplitude 10V (20V peak-to-peak) and frequency 250Hz. Draw both the input and output. (10 pts)

