

ExamPle

Example of a 285 Final Exam

This is a reasonable exam for ECE285.

Due 12/13. Students successfully completing this exam and turning it in on Friday, 12/13, will receive extra-credit.

While during the real exam there won't be any consulting of notes or friends, for the purposes of this ExamPle it is *fair* to use your notes, ask questions of your friends about strategies, use calculators and books. In case you want extra-credit for doing this exam, it is **UNFAIR** to check your answers with your friends. Think on your own about the multiple choice questions (1 to 6) and the concepts questions (12 and 13).

Question	Max points	Grade
1	2	
2	2	
3	2	
4	2	
5	1	
6	1	
7	16	
8	16	
9	16	
10	16	
11	16	
12	5	
13	5	
total		


On this exam please assume, unless otherwise specified, that:

- voltages are measured in reference to ground.
- Light bulbs are resistances.
- All switches are actuated in the direction shown by their arrows at $t=0s$, unless otherwise noted by the switch.
- Operational amplifiers are properly powered, so that they usually don't saturate.

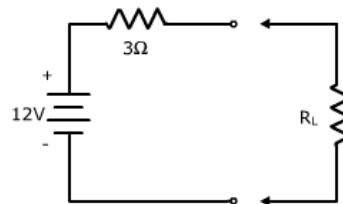1.

**Convert the Thevenin circuit below to a Norton equivalent circuit.
How much is the maximum power the circuit can supply to load resistor R_L ?**

- $I_{Nort} = 9A, R_{Nort} = 9\Omega$ & $P_{max} = 27W$
- $I_{Nort} = 6A, R_{Nort} = 6\Omega$ & $P_{max} = 54W$
- $I_{Nort} = 4A, R_{Nort} = 3\Omega$ & $P_{max} = 12W$




2. A light bulb is connected to a voltage supply and lights up. When a second one is connected in parallel to the first one:

- a) Current through the first one will go up.
- b) Nothing changes, as they are in parallel.
- c) Required power from the supply will stay constant.
- d) Current through the first will go down.
- e) None of the above.

3. If nodes 1 and 3 are shorted:

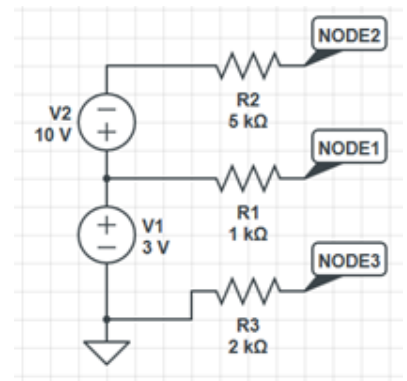- a) The voltage in node 1 (referenced to ground) goes from 3V to 0V.
- b) The voltage across R_1 goes from zero to 1V.
- c) The current through R_1 stays the same.
- d) The voltage across R_2 goes from zero to 10V.
- e) Two or more of the previous statements are true.




4. You are analyzing a circuit on a breadboard. The oscilloscope shows an almost perfect sinewave with 16.67ms period. The most likely scenario is:


- a) The circuit is a sinewave generator.
- b) The circuit isn't working.
- c) The circuit is a notch filter.
- d) The circuit is definitely working.
- e) You pressed "auto setup" on the scope, so it is showing the 60Hz.

5. From the images below, select the summing amplifier:

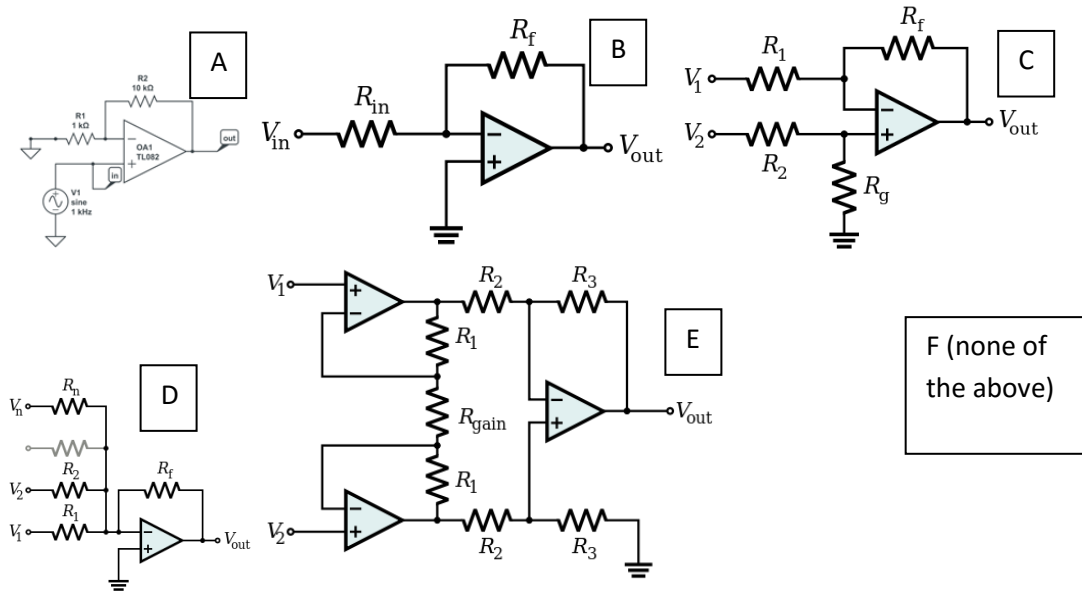
6. From the images below, select the voltage follower:



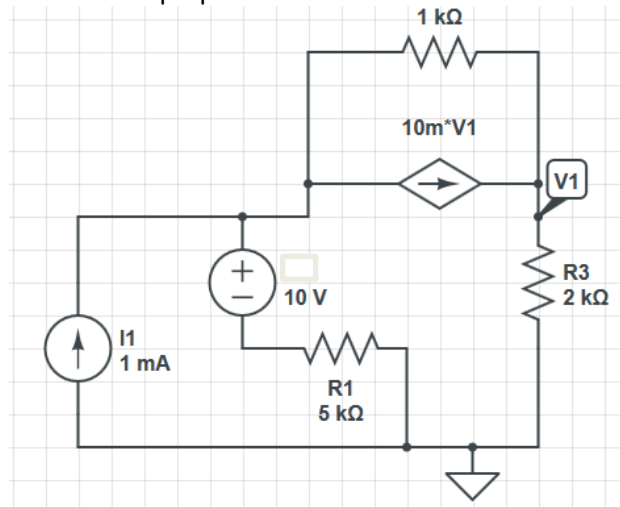
7. Find the current through R3. Indicate the direction. Use superposition.



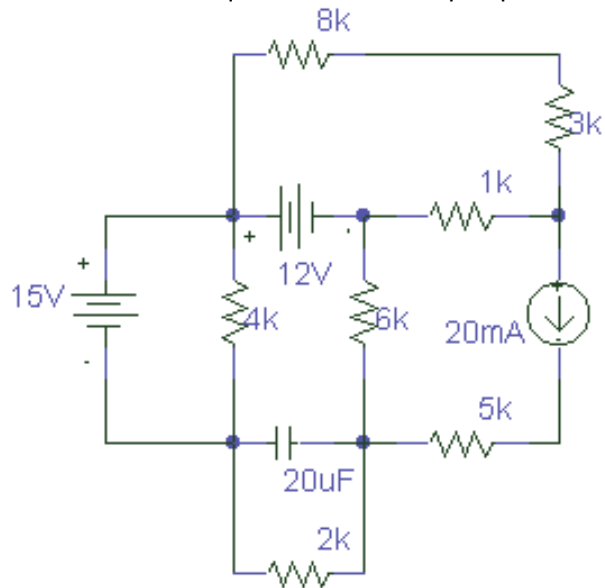8. Find the Norton equivalent from the perspective of the 20uF capacitor.



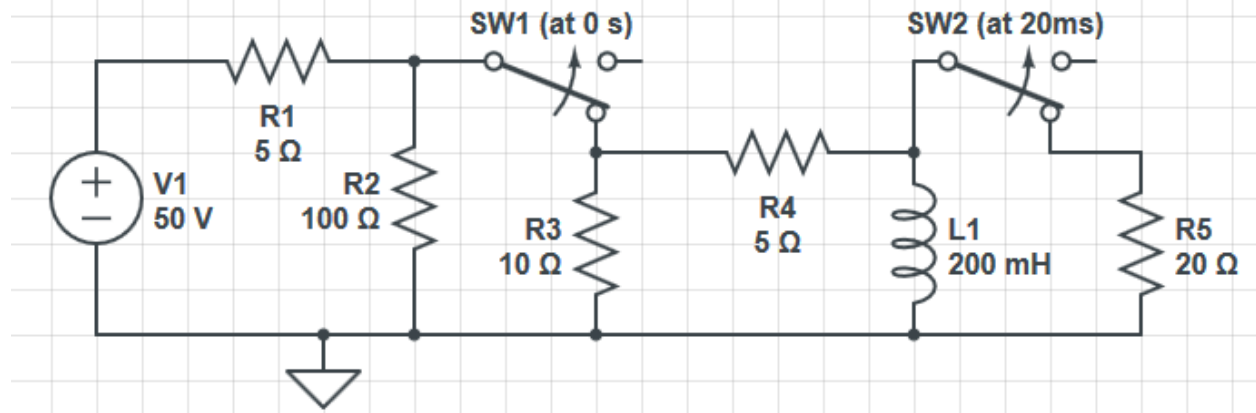9. (a) Find the voltage across the inductor over time.
 (b) What is the voltage on the left terminal of the SW2 (switch 2, which opens at 20ms) at $t=10\text{s}$? ___



10. Find the voltage across C1 and sketch it out (the sketch needs to contain time marks and voltage marks on the axes). At what time does the capacitor have 33% of its final voltage?

